

ASSIGNMENT NUMBER: 2

VLSI Design and Technology


Name: SANSKRITI

Faculty Number: 20ELB270



Enrolment Number: GK8667

Serial Number :36

Schematic:

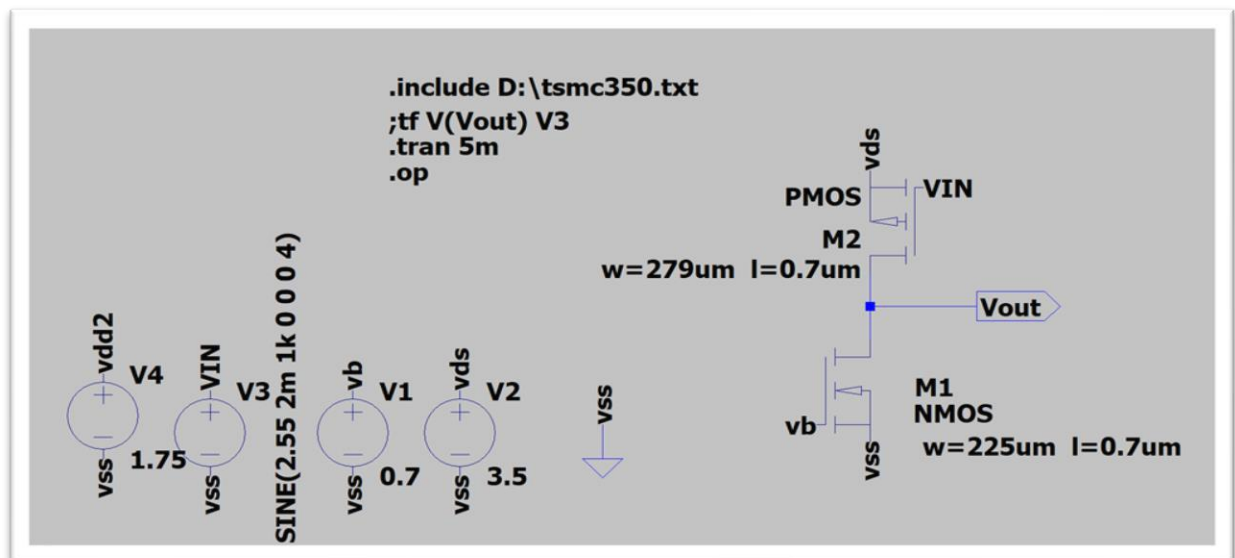

Transient analysis waveform:

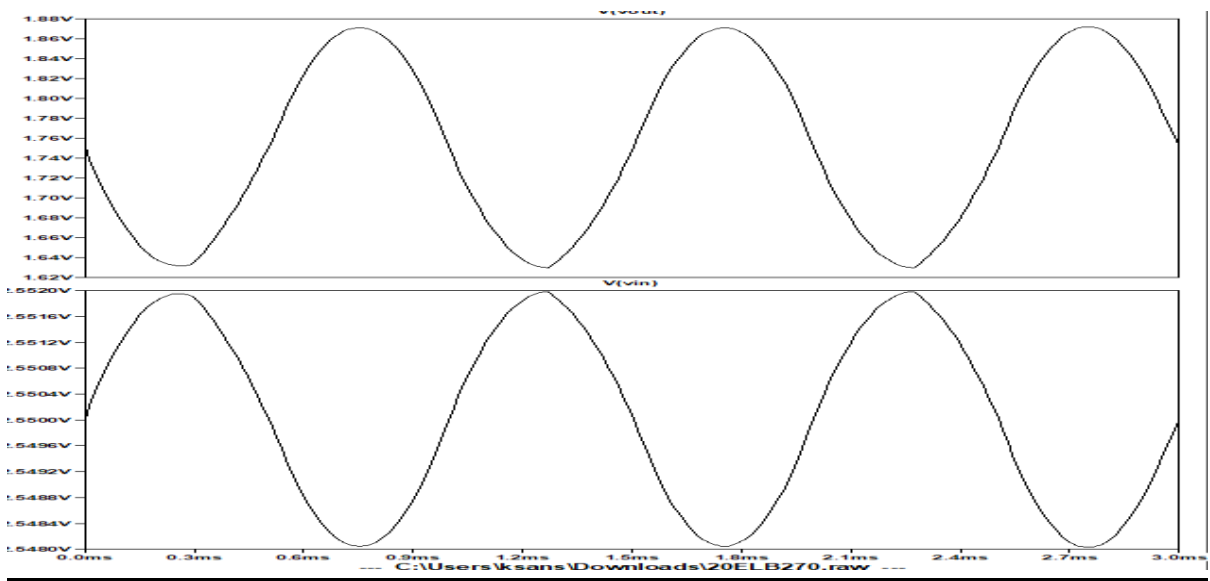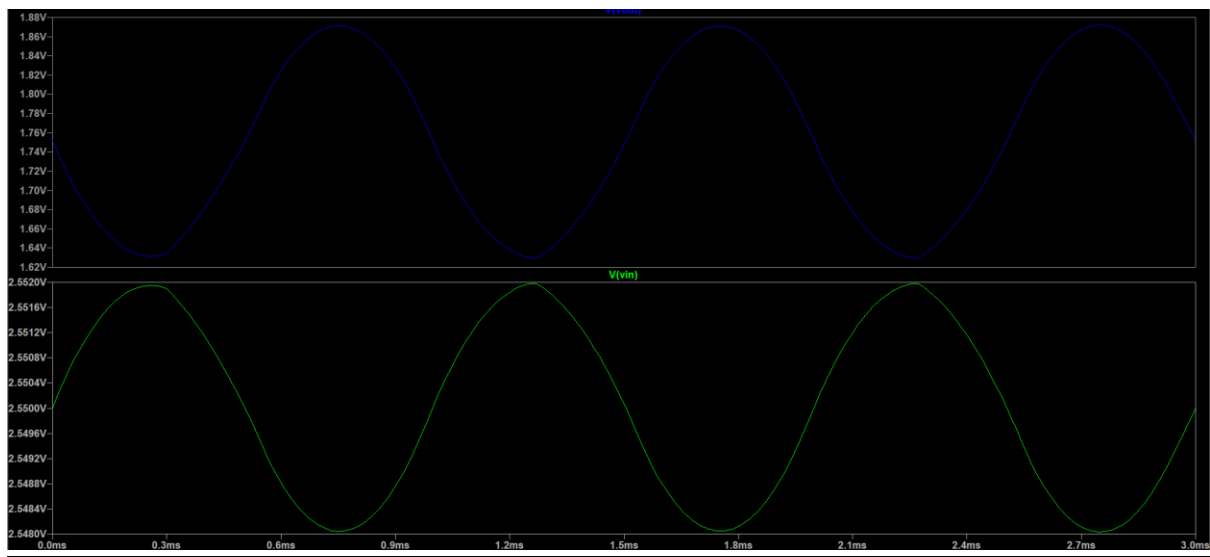

Operation point:

```
* C:\Users\ksans\Downloads\20ELB270.asc
--- Operating Point ---

V(vout):      1.75198      voltage
V(vb):        0.7         voltage
V(vds):       3.5         voltage
V(vin):       2.55        voltage
V(vdd2):      1.75        voltage
Id(M2):       -0.000357997 device_current
Ig(M2):       -0          device_current
Ib(M2):       1.75802e-012 device_current
Is(M2):       0.000357997 device_current
Id(M1):       0.000357997 device_current
Ig(M1):       0          device_current
Ib(M1):       -1.76198e-012 device_current
Is(M1):       -0.000357997 device_current
I(V4):        0          device_current
I(V3):        0          device_current
I(V2):       -0.000357997 device_current
I(V1):        0          device_current
```

```
--- Transfer Function ---

Transfer_function:      -61.3964      transfer
r3#Input_impedance:     1e+020      impedance
output_impedance_at_V(vout): 16106.9      impedance
```